

Capacitor Charging and Discharging

Prof. Ben Varcoe

Room: Bragg 3.16E

<https://calendly.com/b-varcoe/student-meetings>


October 21, 2024

Capacitor Charging

Demonstration: Charging a $100\ \mu\text{F}$ Capacitor

- ▶ We charge a $100\ \mu\text{F}$ capacitor using a 5V source.
- ▶ Then, we will discharge it through an LED.

Charging Circuit

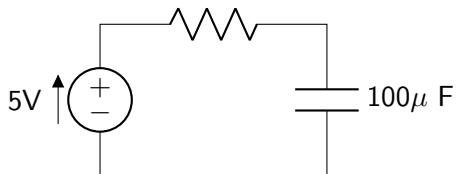


Capacitor Charging


Demonstration: Charging a $100\ \mu\text{F}$ Capacitor

- ▶ We charge a $100\ \mu\text{F}$ capacitor using a 5V source.
- ▶ Then, we will discharge it through an LED.


Charging Circuit

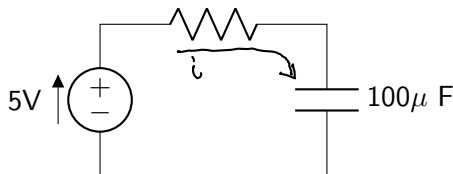


Discharging Circuit

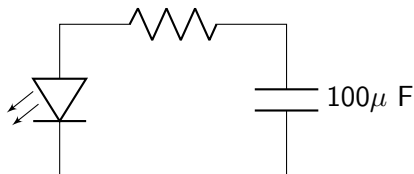

Capacitors in Parallel

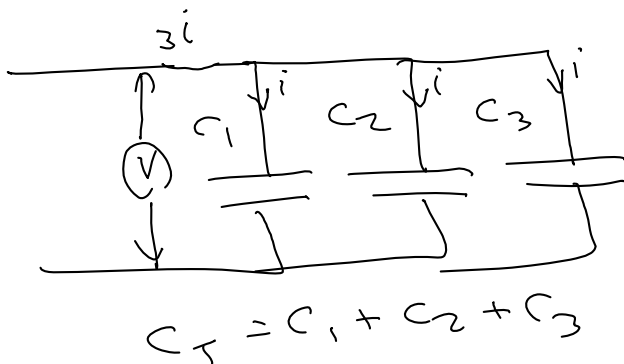

Capacitors in Series

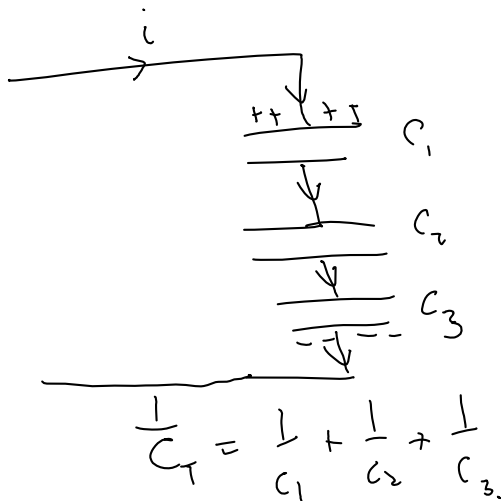

Formula for Capacitor Charging

The voltage across a charging capacitor in an RC circuit is given by:


$$V_C(t) = V_0 \left(1 - e^{-\frac{t}{RC}}\right)$$

The current during the charging process is:

$$I_C(t) = \frac{V_0}{R} e^{-\frac{t}{RC}}$$


Parameters:

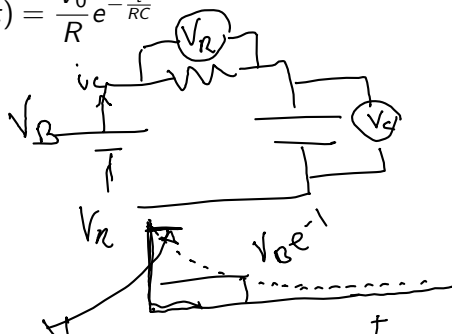- ▶ V_0 : Supply voltage
- ▶ R : Resistance
- ▶ C : Capacitance
- ▶ t : Time



$$V_C = V_B \left(1 - e^{-\frac{t}{RC}}\right)$$

RC - time constant

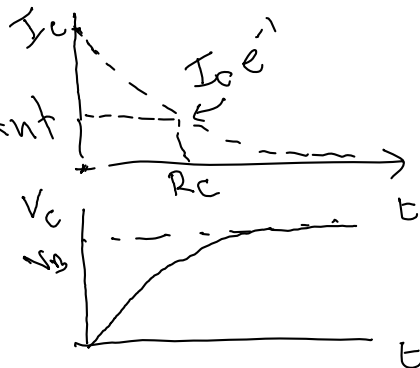

Formula for Capacitor Discharging

The voltage across a discharging capacitor is given by:

$$V_C(t) = V_0 e^{-\frac{t}{RC}}$$

The current during discharging is:

$$I_C(t) = -\frac{V_0}{R} e^{-\frac{t}{RC}}$$


Key Point: Both the voltage and current decay exponentially during discharging.




Demonstration: Measuring Charge/Discharge

Demonstration: Using a Large 100F Capacitor

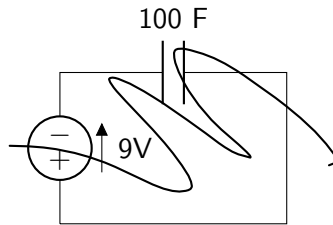- ▶ We will charge a large 100F capacitor.
- ▶ The long charge/discharge time will allow real-time measurement.
- ▶ We will use a digital multimeter (DMM) to track the voltage.



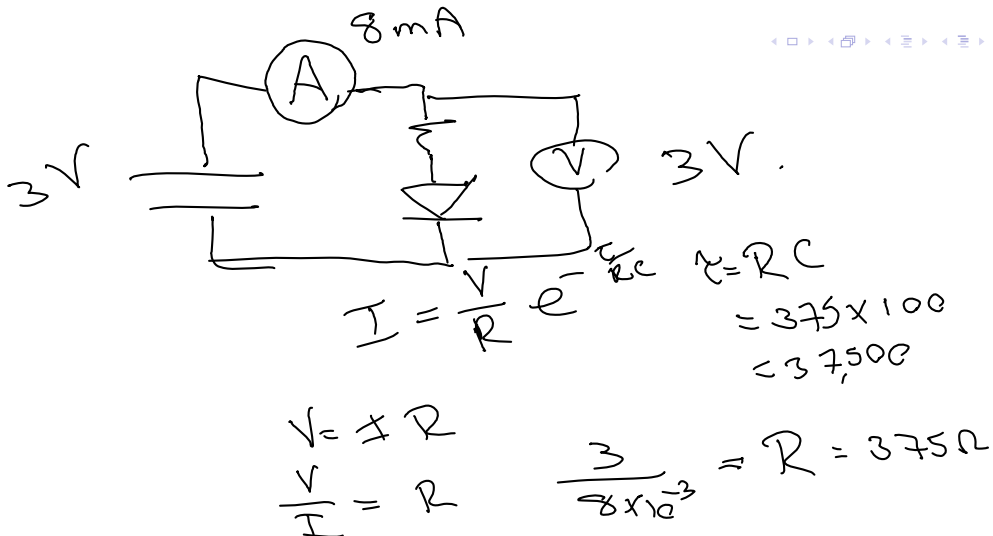Observe: The slow discharge can be measured and observed using the DMM in real time.



Key Takeaways

- ▶ Capacitors store electrical energy and release it over time.
- ▶ Parallel capacitors increase total capacitance, leading to longer discharge times.
- ▶ The charging and discharging behavior is governed by exponential functions.
- ▶ Demonstrations helped us visualize these concepts with real-time measurements.

Energy Storage in a Capacitor

- ▶ A capacitor stores energy in the form of an electric field between its plates.
- ▶ The energy stored in a capacitor is related to the charge Q on the plates and the voltage V across the capacitor.
- ▶ The energy stored in a capacitor is given by:

$$E_C = \frac{1}{2} CV^2$$

$$50 \times 9 \approx 450 \text{ J}$$

where:

- ▶ E_C is the energy stored (in joules),
- ▶ C is the capacitance (in farads),
- ▶ V is the voltage across the capacitor (in volts).

Key Concept

The capacitor stores energy when charged, and this energy is released when the capacitor discharges.

Inductors in Circuits

- ▶ An inductor opposes changes in current by storing energy in its magnetic field.
- ▶ Voltage across an inductor is proportional to the rate of change of current:


$$V_L = L \frac{di}{dt}$$

where L is the inductance and $i(t)$ is the current.

- ▶ Inductors store energy when a current flows through them.


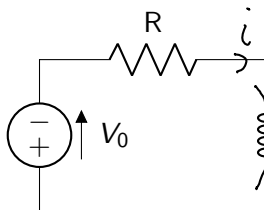
$$\begin{aligned} IR &= -L \frac{dI}{dt} \\ \frac{R}{L} I &= \frac{dI}{dt} \end{aligned}$$



$$V_L = L \frac{dI}{dt}$$

↑
Inductance

Navigation icons: back, forward, search, etc.

if $I = e^{-at}$

$$\frac{R}{L} e^{-at} = -a e^{-at}$$

$$a = \frac{R}{L}$$

Time constant

$$I_L = I_0 e^{-\frac{Rt}{L}}$$

Energy Stored in an Inductor

- ▶ When a current $i(t)$ flows through an inductor, energy is stored in its magnetic field.
- ▶ The energy stored is given by:

$$E_L = \frac{1}{2}Li(t)^2$$

- ▶ This energy is released when the current decreases.

Key Points


- ▶ Energy storage in inductors is analogous to energy storage in capacitors.
- ▶ Inductors resist changes in current (unlike capacitors, which resist changes in voltage).

Charging an Inductor

- ▶ Consider an RL circuit with a resistor R , an inductor L , and a DC voltage source V_0 .
- ▶ Kirchhoff's Voltage Law (KVL) applied to the loop gives:

$$V_0 = V_R + V_L = i(t)R + L \frac{di}{dt}$$

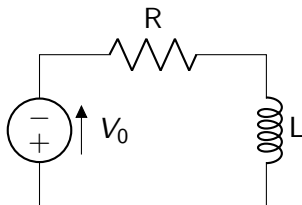- ▶ This differential equation governs the charging process of the inductor.



Solving the Inductor Charging Equation

- ▶ From KVL:

$$V_0 = i(t)R + L \frac{di}{dt}$$

Rearrange:

$$\frac{di}{dt} = \frac{V_0 - i(t)R}{L}$$

- ▶ Solving this gives the current as a function of time:

$$i(t) = \frac{V_0}{R} \left(1 - e^{-\frac{R}{L}t} \right)$$

Energy Stored During Charging

- ▶ As current builds up in the inductor, energy is stored in its magnetic field.
- ▶ The energy stored at any time t is:

$$E_L = \frac{1}{2}Li(t)^2$$

- ▶ At steady state ($t \rightarrow \infty$), the current reaches $i_\infty = \frac{V_0}{R}$, and the maximum energy stored is:

$$E_{L,\max} = \frac{1}{2}L \left(\frac{V_0}{R} \right)^2$$

Example Problem: Inductor Charging

- ▶ Given a circuit with $V_0 = 12\text{ V}$, $R = 10\ \Omega$, and $L = 5\text{ H}$:
- ▶ Find the current $i(t)$ at $t = 2\text{ s}$.

$$i(t) = \frac{V_0}{R} \left(1 - e^{-\frac{R}{L}t} \right)$$

Example Problem: Inductor Charging

- ▶ Given a circuit with $V_0 = 12\text{ V}$, $R = 10\ \Omega$, and $L = 5\text{ H}$:
- ▶ Find the current $i(t)$ at $t = 2\text{ s}$.

$$i(t) = \frac{V_0}{R} \left(1 - e^{-\frac{R}{L}t}\right)$$

$$i(2) = \frac{12}{10} \left(1 - e^{-\frac{10}{5} \times 2}\right) = 1.2\text{ A}$$