

## Chapter 3: Solid State Switching

### 1 Lecture 8: Introduction to Diodes

#### 1.1 Diode Fundamentals and IV Characteristics

A diode is a two-terminal device that allows current to flow primarily in one direction. Its operation is based on the properties of a **PN junction**, formed by joining p-type and n-type semiconductors.

##### 1.1.1 Forward Bias

When the p-side is connected to a positive voltage and the n-side to a negative voltage:

- The depletion region narrows as electrons and holes recombine.
- A forward current flows if the applied voltage exceeds the **threshold voltage** (approximately 0.7 V for silicon diodes and 0.3 V for germanium diodes).

##### 1.1.2 Reverse Bias

When the p-side is connected to a negative voltage and the n-side to a positive voltage:

- The depletion region widens, inhibiting current flow.
- A small **reverse saturation current** flows due to minority carriers.
- If the reverse voltage exceeds the **breakdown voltage**, significant current can flow, potentially damaging the diode (unless designed as a Zener diode).

##### 1.1.3 IV Characteristics

The relationship between current ( $I$ ) and voltage ( $V$ ) for a diode is given by:

$$I = I_s \left( e^{\frac{V}{nV_T}} - 1 \right)$$

where:

- $I_s$ : Saturation current (typically very small).
- $V_T$ : Thermal voltage ( $\sim 26$  mV at room temperature).
- $n$ : Ideality factor ( $n \approx 1$  for ideal diodes).

## 1.2 Rectification and Applications

### 1.2.1 Half-Wave Rectifier

- Consists of a single diode.
- Converts AC to pulsating DC by allowing only the positive half-cycle of the AC waveform to pass.
- Output RMS voltage is approximately  $V_{\text{peak}}/\sqrt{2}$ .

### 1.2.2 Full-Wave Bridge Rectifier

- Utilizes four diodes in a bridge configuration.
- Converts both halves of the AC waveform into pulsating DC.
- Often paired with a capacitor to smooth the output, reducing ripple voltage.

## 1.3 Zener Diodes and Voltage Regulation

Zener diodes are designed to operate in the reverse breakdown region. They are used in circuits to:

- Provide a stable reference voltage.
- Regulate voltage by clamping excess voltage in a circuit.

## 1.4 Example Problems

### 1.4.1 Problem 1: IV Characteristics

**Problem:** Plot the IV curve of a silicon diode with:

- $V = 0.8$  V,  $I_s = 10^{-12}$  A.
- $n = 1.2$ ,  $V_T = 26$  mV.

**Solution:** Using the diode equation:

$$I = 10^{-12} \left( e^{\frac{0.8}{1.2 \cdot 0.026}} - 1 \right)$$

#### 1.4.2 Problem 2: Full-Wave Rectifier

**Problem:** For an AC input voltage of  $V_{\text{in}} = 10 V_{\text{peak}}$ :

- Calculate the RMS output voltage.
- Determine the frequency of the rectified signal ( $f_{\text{in}} = 60 \text{ Hz}$ ).

**Solution:**

- RMS Output Voltage:  $V_{\text{out,RMS}} = V_{\text{peak}}/\sqrt{2}$ .
- Frequency:  $f_{\text{out}} = 2 \cdot f_{\text{in}}$ .

#### 1.4.3 Problem 3: Zener Voltage Regulation

**Problem:** A 6.2 V Zener diode regulates a 12 V supply with a 1 k $\Omega$  resistor:

- Calculate the current through the Zener diode.
- Determine the maximum load resistance maintaining regulation.

**Solution:**

- Zener current:  $I_Z = (12 - 6.2)/1000$ .
- Maximum load current:  $I_{\text{load}} = I_Z - I_{\text{min}}$ .

### 1.5 Summary

- Diodes are essential components enabling unidirectional current flow.
- Applications include rectification, clamping, and voltage regulation.
- Zener diodes are critical for maintaining a stable reference voltage in circuits.