

Lecture 4: AC Circuits and Impedance

Prof. Ben Varcoe

Room: Bragg 3.16E

<https://calendly.com/b-varcoe/student-meetings>

October 24, 2024


Introduction to AC Circuits

In Alternating Current (AC) circuits, the current and voltage vary sinusoidally over time. A typical AC voltage source can be expressed as:


$$V(t) = V_0 \sin(\omega t)$$

where:

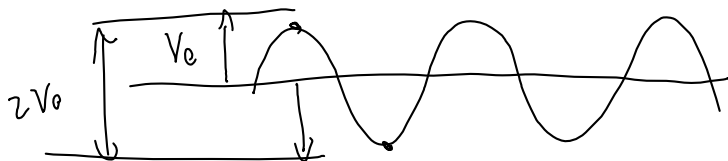- ▶ V_0 is the peak voltage (maximum amplitude),
- ▶ ω is the angular frequency in radians per second ($\omega = 2\pi f$, where f is the frequency in Hz),
- ▶ t is the time in seconds.




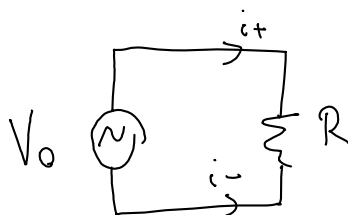Navigation icons: back, forward, search, etc.



how do we
calculate the
power lost
in the resistor?
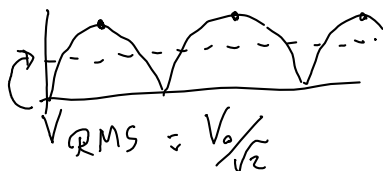
$$\begin{aligned} P &= I^2 R \\ &= VI \\ &= \frac{V^2}{R} \end{aligned}$$



Introduction to AC Circuits

In Alternating Current (AC) circuits, the current and voltage vary sinusoidally over time. A typical AC voltage source can be expressed as:

$$V(t) = V_0 \sin(\omega t)$$

where:

- ▶ V_0 is the peak voltage (maximum amplitude),
- ▶ ω is the angular frequency in radians per second ($\omega = 2\pi f$, where f is the frequency in Hz),
- ▶ t is the time in seconds.

The root-mean-square (RMS) value of the voltage is given by:

$$V_{\text{RMS}} = \frac{V_0}{\sqrt{2}}$$

Do it Yourself: AC Voltage and Frequency

Exercise:

Given an AC source with a peak-to-peak voltage of 680V and a frequency of 50Hz:

1. Write the equation for $V(t)$. $= V_0 \sin(\omega t)$

2. Calculate the RMS voltage.

$$= \frac{680}{2} \sin(100\pi t)$$
$$V_{RMS} = 240V.$$

Inductors and Capacitors: Opposition to Change

Key Concepts:

- ▶ Inductors oppose changes in **current**.
- ▶ Capacitors oppose changes in **voltage**.

Equations:

Capacitor	Inductor
$i = C \frac{dV}{dt}$	$v = L \frac{di}{dt}$

$$\frac{V}{R} \approx C \frac{dV}{dt}$$
$$\frac{1}{RC} V = \frac{dV}{dt}$$

guess $V = e^{-\frac{t}{\tau}} e$

$$\tau \approx RC$$

$$IR \approx L \frac{dI}{dt}$$


Inductors and Capacitors: Opposition to Change

Key Concepts:

- ▶ Inductors oppose changes in **current**.
- ▶ Capacitors oppose changes in **voltage**.

Equations:


Capacitor	Inductor
$i = C \frac{dV}{dt}$	$v = L \frac{di}{dt}$
Constant voltage \Rightarrow Zero current	Constant current \Rightarrow <u>Zero voltage</u>

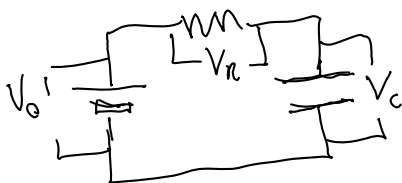

$$V_C = V_0$$

$$V_R = 0$$

$$I = 0$$

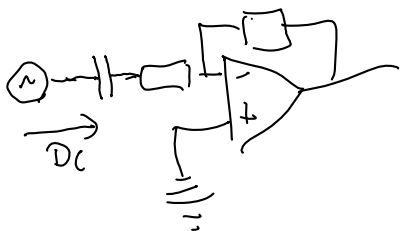

Navigation icons: back, forward, search, etc.

$$V_L = 0$$

$$V_R = V_0$$

$$I = \frac{V_0}{R}$$



Inductors and Capacitors: Opposition to Change

Key Concepts:

- ▶ Inductors oppose changes in **current**.
- ▶ Capacitors oppose changes in **voltage**.

Equations:

Capacitor	Inductor
$i = C \frac{dV}{dt}$	$v = L \frac{di}{dt}$
Constant voltage \Rightarrow Zero current	Constant current \Rightarrow Zero voltage
Passes High Frequency	Blocks High Frequency

Inductors and Capacitors: Opposition to Change

Key Concepts:


- ▶ Inductors oppose changes in **current**.
- ▶ Capacitors oppose changes in **voltage**.

Equations:


Capacitor	Inductor
$i = C \frac{dV}{dt}$	$v = L \frac{di}{dt}$
Constant voltage \Rightarrow Zero current	Constant current \Rightarrow Zero voltage
Passes High Frequency	Blocks High Frequency
reactance: $X_c = \frac{1}{j\omega C} = \frac{-j}{\omega C}$	reactance: $X_L = j\omega L$

$$X_c = \frac{1}{j\omega C}$$

Impedance in RLC Circuits

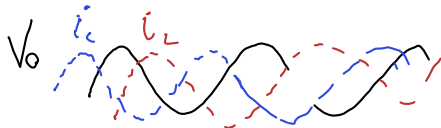

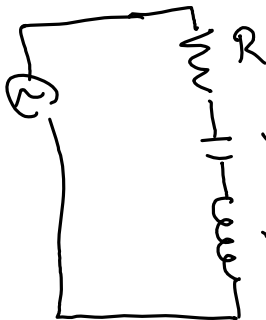reactance: $X_C = \frac{1}{j\omega C} = \frac{-j}{\omega C}$, $X_L = \underline{j\omega L}$



$$X_C = \frac{-j}{\omega C}$$

$$X_L = j\omega L$$

$$X_{LC} = X_C + X_L$$

$$= j\omega L - \frac{j}{\omega C}$$

$$= j\left(\omega L - \frac{1}{\omega C}\right)$$

$$X = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

$$\text{Impedance} \Rightarrow Z = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

Impedance in RLC Circuits

reactance: $X_C = \frac{1}{j\omega C} = \frac{-j}{\omega C}$ reactance: $X_L = j\omega L$

Impedance in RLC Circuits

reactance: $X_C = \frac{1}{j\omega C} = \frac{-j}{\omega C}$ reactance: $X_L = j\omega L$

Impedance, denoted by Z , is the total opposition to current flow in an AC circuit. The impedance of a series RLC circuit is given by:

$$Z = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

where:

- ▶ R is the resistance in ohms (Ω),
- ▶ L is the inductance in henrys (H),
- ▶ C is the capacitance in farads (F),
- ▶ ω is the angular frequency of the AC source.

Do it Yourself: Impedance Calculation

Exercise:

For a series RLC circuit with:

$$R = 50 \, \Omega, \quad L = 0.2 \, \text{H}, \quad C = 20 \, \mu\text{F}, \quad f = 60 \, \text{Hz}$$

1. Calculate inductive reactance X_L and capacitive reactance X_C .
2. Determine the total impedance Z .

Resonance and Bandwidth

Resonance and Bandwidth

Resonance occurs when the inductive reactance X_L and capacitive reactance X_C cancel each other out, i.e.,

$$\omega L = \frac{1}{\omega C}$$

At resonance, the impedance of the circuit is purely resistive ($Z = R$) and the resonant frequency is given by:

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

Do it Yourself: Resonant Frequency

Exercise:

For a series RLC circuit with:

$$L = 1 \text{ H}, \quad C = 100 \mu\text{F}$$

Calculate the resonant frequency f_0 .

Example 1: Series RLC Circuit with Sinusoidal Input

Consider a series RLC circuit with:

$$R = 10\ \Omega, \quad L = 0.1\ \text{H}, \quad C = 100\ \mu\text{F}$$

The circuit is driven by a sinusoidal voltage source

$$V(t) = 50 \sin(1000t).$$

Task:

- ▶ Calculate the total impedance.
- ▶ Find the current in the circuit.

Solution

Reactance of each component:

Solution

Reactance of each component:

$$Z_R = 10 \, \Omega, \quad X_L = j100 \, \Omega, \quad X_C = -j10 \, \Omega$$

Total reactance:

Solution

Reactance of each component:

$$Z_R = 10 \, \Omega, \quad X_L = j100 \, \Omega, \quad X_C = -j10 \, \Omega$$

Total reactance:

$$Z_{\text{total}} = Z_R + X_L + X_C = 10 + j90 \, \Omega$$

Magnitude of impedance:

Solution

Reactance of each component:

$$Z_R = 10 \, \Omega, \quad X_L = j100 \, \Omega, \quad X_C = -j10 \, \Omega$$

Total reactance:

$$Z_{\text{total}} = Z_R + X_L + X_C = 10 + j90 \, \Omega$$

Magnitude of impedance:

$$|Z_{\text{total}}| = \sqrt{10^2 + 90^2} = 90.55 \, \Omega$$

Current in the circuit:

Solution

Reactance of each component:

$$Z_R = 10 \, \Omega, \quad X_L = j100 \, \Omega, \quad X_C = -j10 \, \Omega$$

Total reactance:

$$Z_{\text{total}} = Z_R + X_L + X_C = 10 + j90 \, \Omega$$

Magnitude of impedance:

$$|Z_{\text{total}}| = \sqrt{10^2 + 90^2} = 90.55 \, \Omega$$

Current in the circuit:

$$I(t) = \frac{V(t)}{|Z_{\text{total}}|} = 0.552 \sin(1000t) \, \text{A}$$

Applications of AC Circuits

- ▶ **Power Distribution:** AC is used in power systems for ease of voltage transformation.
- ▶ **Tuned Circuits:** RLC circuits are used in communication systems for tuning to specific frequencies.
- ▶ **Filters:** AC circuits with capacitors and inductors filter unwanted frequencies in signal processing.